

Como conectar un pulsador

(sin abrir un portal al Multiverso... otra vez)




¿Qué es un pulsador?

Es un **interruptor momentáneo**.
Solo se **activa** cuando es **presionado**.

Sirve para activar o desactivar algo en el circuito.




¿Qué es un pulsador?

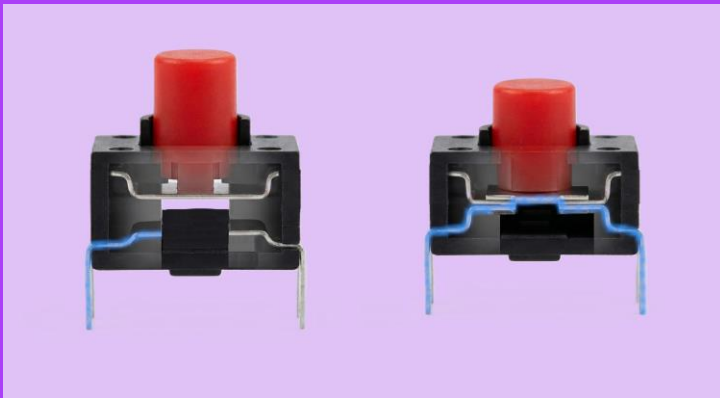

Por dentro, **dos de sus patitas están separadas**, cuando es presionado se unen y dejan pasar la electricidad.

¿Qué es un pulsador?


No presionado.

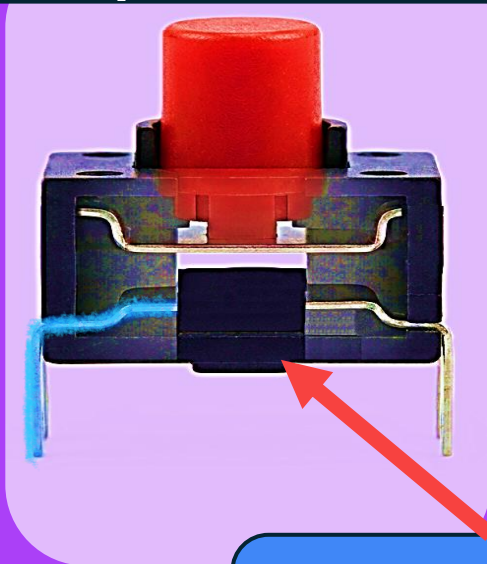

No pasa la
electricidad.



Presionado.

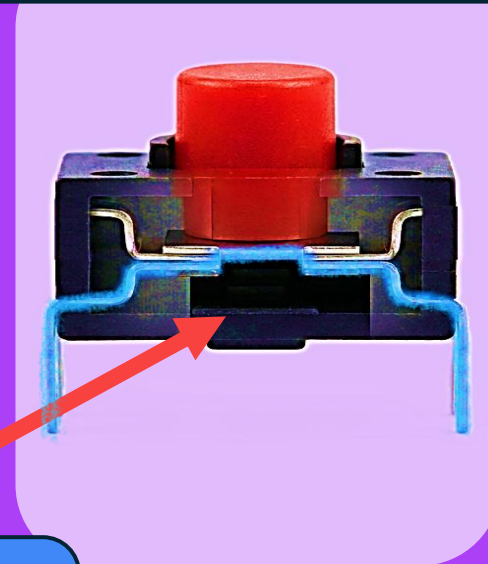

Sí pasa la
electricidad.



¿¿Cómo saber que patitas
utilizar??



¿Cómo saber que patitas utilizar?




Lo volteamos y buscamos una **división**.

Las patitas que están en **lados diferentes de la división** son las patitas que están **separadas por dentro**.

Esas son las que utilizaremos.


¿Cómo saber que patitas utilizar?

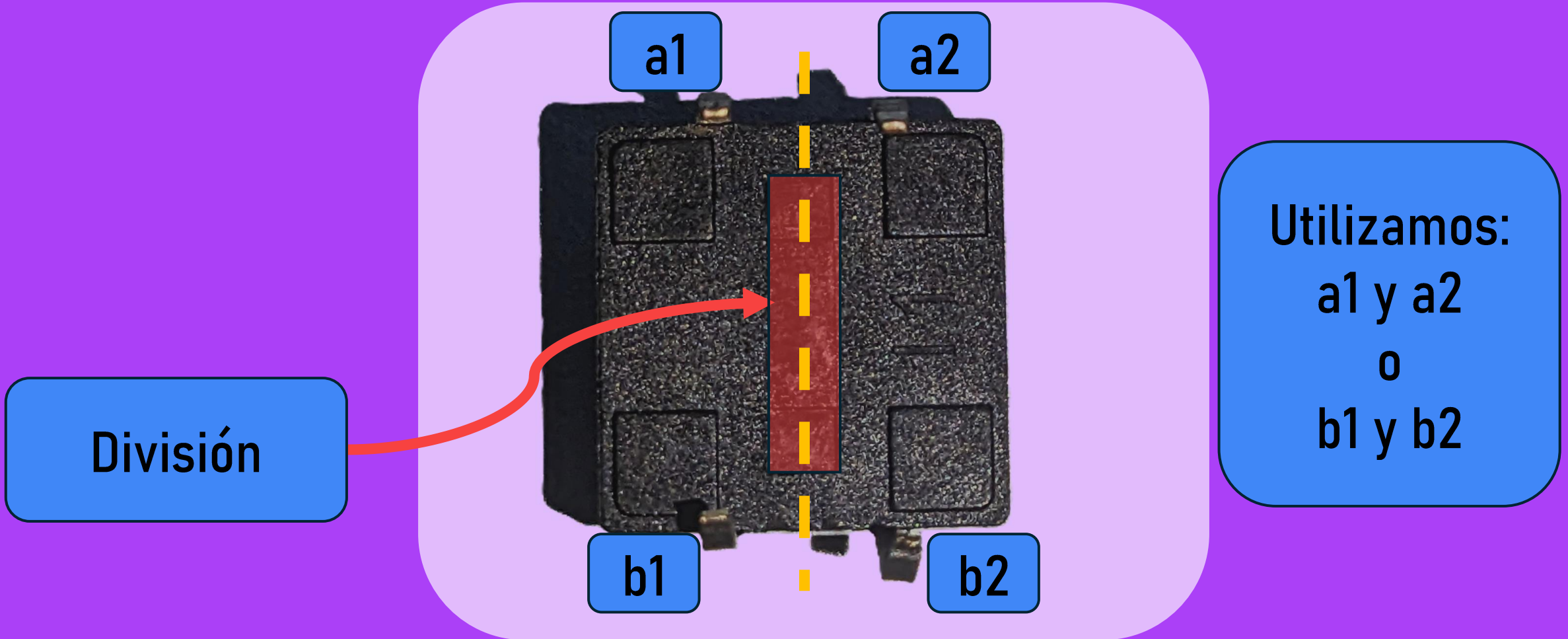

The background is a solid light purple color. It features several abstract, organic shapes in various shades of blue, teal, and orange. A large, irregular orange shape is in the top left corner. A smaller, light blue shape is in the top center. A large, irregular blue shape is in the top right corner. A small, light blue shape is in the bottom right corner. A large, irregular orange shape is in the bottom left corner.

Conexiones

La más básica

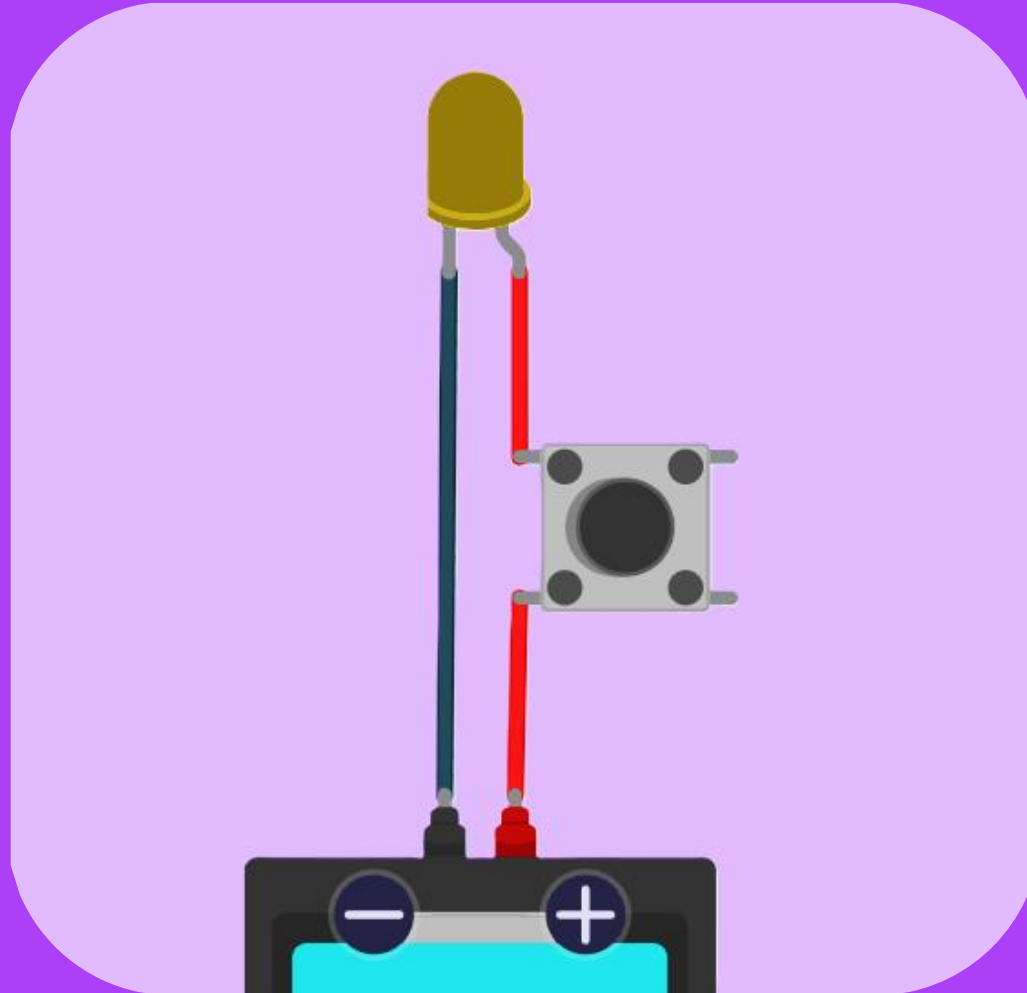

En Protoboard

